

**CSE477**  
**VLSI Digital Circuits**  
**Fall 2002**

**Lecture 26: Low Power Techniques in Microarchitectures and Memories**

Mary Jane Irwin ( [www.cse.psu.edu/~mji](http://www.cse.psu.edu/~mji) )  
[www.cse.psu.edu/~cg477](http://www.cse.psu.edu/~cg477)

[Adapted from Rabaey's *Digital Integrated Circuits*, ©2002, J. Rabaey et al.]

---

---

---

---

---

---

---

---

**Review: Energy & Power Equations**

$$E = C_L V_{DD}^2 P_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} P_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

$$f_{0 \rightarrow 1} = P_{0 \rightarrow 1} * f_{clock}$$

$$P = C_L V_{DD}^2 f_{0 \rightarrow 1} + t_{sc} V_{DD} I_{peak} f_{0 \rightarrow 1} + V_{DD} I_{leakage}$$

Dynamic power  
 (~90% today and  
 decreasing  
 relatively)

Short-circuit  
 power  
 (~8% today and  
 decreasing  
 absolutely)

Leakage power  
 (~2% today and  
 increasing)

---

---

---

---

---

---

---

---

**Power and Energy Design Space**

	Constant Throughput/Latency	Variable Throughput/Latency
Energy		

---

---

---

---

---


---

---

---
 
### Bus Multiplexing

- Buses are a significant source of power dissipation due to high switching activities and large capacitive loading
  - 15% of total power in Alpha 21064
  - 30% of total power in Intel 80386
- Share long data buses with time multiplexing ( $S_1$  uses even cycles,  $S_2$  odd)



- But what if data samples are correlated (e.g., sign bits)?

---

---

---

---


---

---

---

---

### Correlated Data Streams

 

- For a shared (multiplexed) bus advantages of data correlation are lost (bus carries samples from two uncorrelated data streams)
  - Bus sharing should not be used for **positively** correlated data streams
  - Bus sharing may prove advantageous in a **negatively** correlated data stream (where successive samples switch sign bits) - more random switching

---

---

---

---

---


---

---

---
 
### Glitch Reduction by Pipelining

- Glitches depend on the **logic depth** of the circuit - gates deeper in the logic network are more prone to glitching
  - arrival times of the gate inputs are more spread due to delay imbalances
  - usually affected more by primary input switching
- Reduce logic depth by adding pipeline registers
  - additional energy used by the clock and pipeline registers




---

---

---

---

---

---

---

---

## Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced $V_{dd}$ Sizing Multi- $V_{dd}$	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- $V_T$	Sleep Transistors Multi- $V_{dd}$ Variable $V_T$	+ Variable $V_T$

CSE477 L26 System Power.7

Irwin&Wijay, PSU, 2002

---

---

---

---

---

---

---


---

## Clock Gating

- Most popular method for power reduction of clock signals and functional units

- Gate off clock to idle functional units

 - e.g., floating point units
- need logic to generate **disable** signal
  - increases complexity of control logic
  - consumes power
  - timing critical to avoid clock glitches at OR gate output
- additional gate delay on clock signal
  - gating OR gate can replace a buffer in the clock distribution tree



CSE477 L26 System Power.8

Irwin&Wijay, PSU, 2002

---

---

---

---

---


---

---

---
 
## Clock Gating in a Pipelined Datapath

- For idle units (e.g., floating point units in Exec stage, WB stage for instructions with no write back operation)



CSE477 L26 System Power.9

Irwin&Wijay, PSU, 2002

---

---

---

---

---

---

---

---

## Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced $V_{dd}$ Sizing Multi- $V_{dd}$	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- $V_T$	Sleep Transistors Multi- $V_{dd}$ Variable $V_T$	+ Variable $V_T$

CSE477 L26 System Power.10

Irwin&Vijay, PSU, 2002

---

---

---

---

---

---

---


---

---

---
 
## Review: Dynamic Power as a Function of $V_{DD}$

- Decreasing the  $V_{DD}$  **decreases** dynamic energy consumption (quadratically)
- But, **increases** gate delay (decreases performance)



- Determine the critical path(s) at **design time** and use high  $V_{DD}$  for the transistors on those paths for speed. Use a lower  $V_{DD}$  on the other logic to reduce dynamic energy consumption.

CSE477 L26 System Power.11

Irwin&Vijay, PSU, 2002

---

---

---

---

---

---

---

---

---

---

## Dynamic Frequency and Voltage Scaling

- Intel's SpeedStep
  - Hardware that steps down the clock frequency (dynamic frequency scaling – DFS) when the user unplugs from AC power
    - PLL from 650MHz → 500MHz
  - CPU stalls during SpeedStep adjustment
- Transmeta LongRun
  - Hardware that applies **both DFS and DVS** (dynamic supply voltage scaling)
    - 32 levels of  $V_{DD}$  from 1.1V to 1.6V
    - PLL from 200MHz → 700MHz in increments of 33MHz
  - Triggered when CPU load change is detected by software
    - heavier load → ramp up  $V_{DD}$ , when stable speed up clock
    - lighter load → slow down clock, when PLL locks onto new rate, ramp down  $V_{DD}$
  - CPU stalls only during PLL relock (< 20 microsec)

CSE477 L26 System Power.12

Irwin&Vijay, PSU, 2002

---

---

---

---

---

---

---

---

---

---

## Dynamic Thermal Management (DTM)



Trigger Mechanism:  
When do we enable  
DTM techniques?



Initiation Mechanism:  
How do we enable  
technique?



Response Mechanism:  
What technique do we  
enable?

CSE477 L26 System Power.13

Irwin&Wijay, PSU, 2002

---

---

---

---

---

---

---

---

## DTM Trigger Mechanisms



- Mechanism: How to deduce temperature?
- Direct approach: on-chip temperature sensors
  - Based on differential voltage change across 2 diodes of different sizes
  - May require >1 sensor
  - Hysteresis and delay are problems
- Policy: When to begin responding?
  - Trigger level set too high means higher packaging costs
  - Trigger level set too low means frequent triggering and loss in performance
- Choose trigger level to exploit difference between average and worst case power

CSE477 L26 System Power.14

Irwin&Wijay, PSU, 2002

---

---

---

---

---

---

---

---

## DTM Initiation and Response Mechanisms



- Operating system or microarchitectural control?
  - Hardware support can reduce performance penalty by 20-30%
- Initiation of policy incurs some delay
  - When using DVS and/or DFS, much of the performance penalty can be attributed to enabling/disabling overhead
  - Increasing policy delay reduces overhead; smarter initiation techniques would help as well
- Thermal window (100Kcycles+)
  - Larger thermal windows "smooth" short thermal spikes

CSE477 L26 System Power.15

Irwin&Wijay, PSU, 2002

---

---

---

---


---

---

---

---
 
### DTM Activation and Deactivation Cycle



- Initiation Delay – OS interrupt/handler
- Response Delay – Invocation time (e.g., adjust clock)
- Policy Delay – Number of cycles engaged
- Shutoff Delay – Disabling time (e.g., re-adjust clock)

---

---

---

---

---

---


---

---

---

---

### DTM Savings Benefits

 


---

---

---

---

---

---

---

---

---

---

### Power and Energy Design Space

	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced $V_{dd}$ Sizing Multi- $V_{dd}$	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- $V_T$	Sleep Transistors Multi- $V_{dd}$ Variable $V_T$	+ Variable $V_T$

---

---

---

---

---

---


---

---

---

---

**Speculated Power of a 15mm  $\mu$ P**

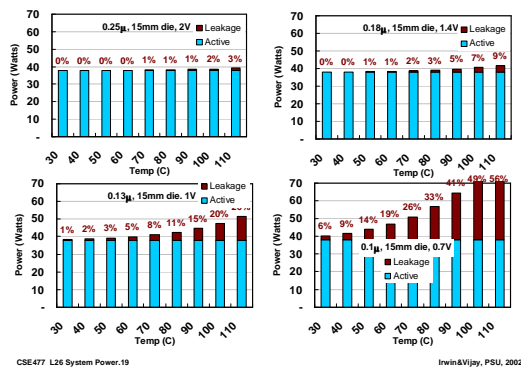


---

---

---

---

---

---

---


---

---

---

 **Review: Leakage as a Function of Design Time V<sub>T</sub>**

- Reducing the V<sub>T</sub> increases the sub-threshold leakage current (exponentially)
- But, reducing V<sub>T</sub> decreases gate delay (increases performance)



- Determine the critical path(s) at design time and use low V<sub>T</sub> devices on the transistors on those paths for speed. Use a high V<sub>T</sub> on the other logic for leakage control.

---

---

---

---

---

---

---

---


---

---

**Review: Variable V<sub>T</sub> (ABB) at Run Time**

□  $V_T = V_{T0} + \gamma(\sqrt{|-2\phi_F + V_{SB}|} - \sqrt{|-2\phi_F|})$   
 where V<sub>T0</sub> is the threshold voltage at V<sub>SB</sub> = 0  
 V<sub>SB</sub> is the source-bulk (substrate) voltage  
 γ is the body-effect coefficient

 - For an n-channel device, the substrate is normally tied to ground
- A negative bias causes V<sub>T</sub> to increase from 0.45V to 0.85V
- Adjusting the substrate bias at run time is called adaptive body-biasing (ABB)




---

---

---

---

---

---

---

---

---

---

## Next Lecture and Reminders

### □ Next lecture

- System level interconnect
  - Reading assignment – Rabaey, et al, xx

### □ Reminders

- Project final reports due December 5<sup>th</sup>
- Final grading negotiations/correction (except for the final exam) must be concluded by December 10<sup>th</sup>
- Final exam scheduled
  - Monday, December 16<sup>th</sup> from 10:10 to noon in 118 and 121 Thomas

---

---

---

---

---

---

---

---